



Skill 40-Ohm's Law

107. An electric circuit consists of a variable resistor connected to a source of constant potential difference. If the resistance of the resistor is doubled, the current through the resistor is

A) halved B) doubled
C) quartered D) quadrupled

$V = IR$
 $I = \frac{V}{R}$ Inverse

108. In a simple electric circuit, a 24-ohm resistor is connected across a 6.0-volt battery. What is the current in the circuit?

A) 1.0 A B) 0.25 A
C) 140 A D) 4.0 A

$R = 24\Omega$
 $V = 6V$
 $I = ?$
 $I = \frac{V}{R} = \frac{6V}{24\Omega}$

109. What is the current in a 100.-ohm resistor connected to a 0.40-volt source of potential difference?

A) 250 mA B) 40. mA
C) 2.5 mA D) 4.0 mA

$I = ?$
 $R = 100\Omega$
 $V = 0.4V$
 $I = \frac{V}{R} = \frac{0.4V}{100\Omega} = 0.004A = 4mA$

110. A 6.0 ohm resistor that obeys Ohm's Law is connected to a source of variable potential difference. When the applied voltage is decreased from 12 V to 6.0 V, the current passing through the resistor

A) remains the same
B) is doubled
C) is halved
D) is quadrupled

V	I	R
12V	2A	6Ω
6V	1A	6Ω

111. In a flashlight, a battery provides a total of 3.0 volts to a bulb. If the flashlight bulb has an operating resistance of 5.0 ohms, the current through the bulb is

A) 0.30 A B) 0.60 A
C) 1.5 A D) 1.7 A

$I = \frac{V}{R} = \frac{3V}{5\Omega} = 0.6A$

112. In a simple electric circuit, a 110-volt electric heater draws 2.0 amperes of current. The resistance of the heater is

A) 0.018 Ω B) 28 Ω
C) 55 Ω D) 220 Ω

$V = 110V$
 $I = 2A$
 $R = ?$
 $R = \frac{V}{I} = \frac{110V}{2A} = 55\Omega$

113. How much current flows through a 12-ohm flashlight bulb operating at 3.0 volts?

A) 0.25 A B) 0.75 A
C) 3.0 A D) 4.0 A

$I = \frac{V}{R} = \frac{3V}{12\Omega} = 0.25A$

114. What is the current through a 25 ohm resistor connected to a 5.0 volt power supply?

A) 0.20 A B) 5.0 A
C) 25 A D) 30. A

$I = \frac{V}{R} = \frac{5V}{25\Omega}$

115. What is the potential difference across a 2.0-ohm resistor that draws 2.0 coulombs of charge per second?

A) 1.0 V B) 2.0 V
C) 3.0 V D) 4.0 V

$V = ?$
 $R = 2\Omega$
 $q = 2C$
 $t = 1s$
 $I = 2A$

$V = IR$
 $= (2A)(2\Omega)$
 $= 4V$

Skill 40-Ohm's Law

116. A 20.-ohm resistor has 40. coulombs passing through it in 5.0 seconds. The potential difference across the resistor is

- A) 8.0 V B) 100 V
 C) 160 V D) 200 V

$R = 20\Omega$
 $Q = 40C$
 $t = 5s$
 $I = 8A$
 $V = IR$
 $V = (8A)(20\Omega) = 160V$

117. The ratio of the potential difference across a conductor to the current in the conductor is called

- A) conductivity B) resistance
 C) charge D) power

$$\frac{V}{I} = R$$

118. If the potential difference across a 12-ohm resistor is 4 volts, the current through the resistor is

- A) 1/3 A B) 1/2 A
 C) 3 A D) 4 A





$V = 4V$
 $R = 12\Omega$
 $I = ?$
 $I = \frac{V}{R} = \frac{4V}{12\Omega} = .33A$

119. A lamp has a current of 2.0 amperes at 6.0 volts. The resistance of the lamp must be

- A) 1.5 Ω B) 6.0 Ω
 C) 3.0 Ω D) 12 Ω

$I = 2A$
 $V = 6V$
 $R = \frac{V}{I} = \frac{6V}{2A} = 3\Omega$

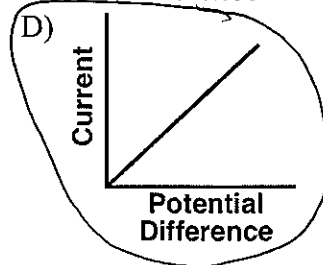
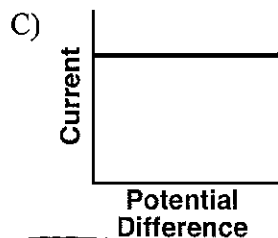
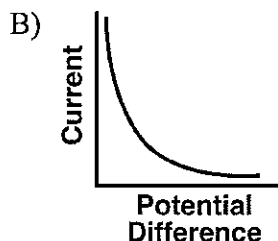
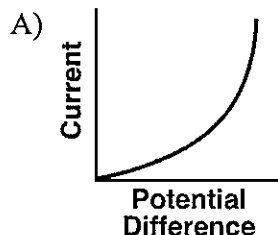
120. The resistance of a circuit remains constant. Which graph best represents the relationship between the current in the circuit and the potential difference provided by the battery?



$$I = \frac{V}{R}$$


Skill 40-Ohm's Law

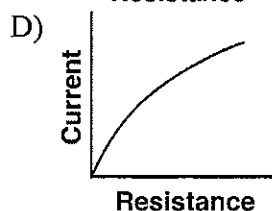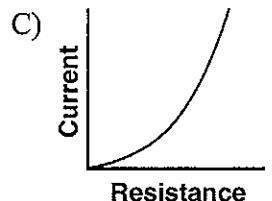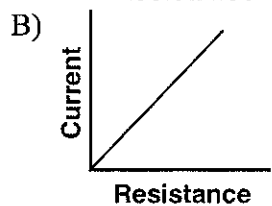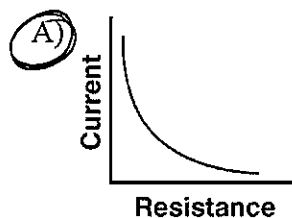121. A constant potential difference is applied across a variable resistor held at constant temperature. Which graph best represents the relationship between the resistance of the variable resistor and the current through it?



$$I = \frac{V}{R}$$

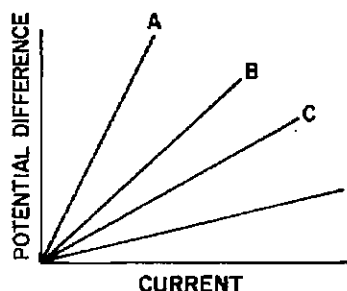122. The graph below shows the relationship between current and potential difference for four resistors A, B, C, and D.




$$\frac{V}{I} = R$$

Slope

Which resistor has the greatest resistance?

- A) A B) B C) C D) D

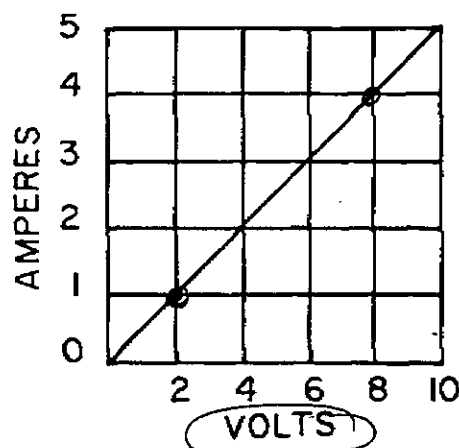123. Base your answer to the following question on the graph below which represents data obtained by applying different potential differences to a metallic conductor at a constant temperature.



$$R = \frac{V}{I}$$


The resistance of the conductor is approximately

- A) 1.0Ω B) 2.0Ω
C) 0.5Ω D) 4.0Ω

$$\frac{8V - 2V}{4A - 1A} = \frac{6V}{3A} = 2 \Omega$$

Skill 40-Ohm's Law

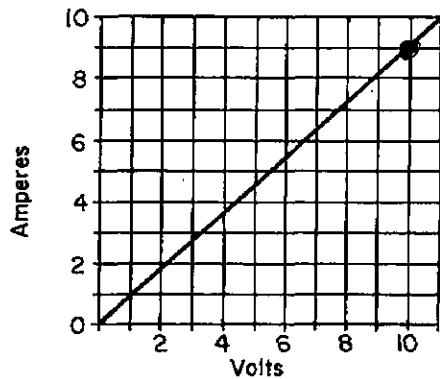124. Base your answer to the following question on the accompanying graph which shows the data collected for a copper wire at a constant temperature.



The resistance of the wire is closest to

- A) $1\ \Omega$ B) $2\ \Omega$
C) $0.5\ \Omega$ D) $4\ \Omega$

$$R = \frac{V}{I}$$